Template Week 2 – Logic

Student number: 569527

Assignment 2.1: Parking lot

Which gates do you need?

AND Gates

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Assignment 2.2: Android/iPhone

Which gates do you need?

XOR GATE

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

Assignment 2.3: Four NAND gates

Complete this table


Α	В	Q
0	0	1
0	1	0
1	0	0
1	1	1

How can the design be simplified?

Instead of using several components to construct such a circuit-four NAND gates in this casethe design can be dramatically simplified by using a single XOR gate. The XOR does the same operation that the four NANDs do, just in a much simpler way. With an XOR gate

Assignment 2.4: Getting to know Logisim evolution

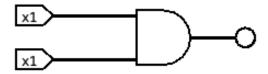Screenshot of the design with your name and student number in it:




Michal Mucha -569527

(in Logisim LED is glowing)

Assignment 2.5: SR Latch

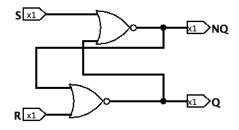
Screenshot SR Latch in Logisim with your name and student number:



Michal Mucha-569527

Assignment 2.6: Vending Machine

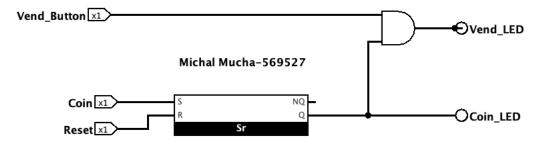Screenshot Vending Machine in Logisim with your name and student number:



Bonus point assignment – week 2

Create a java program that accepts user input and presents a menu with options.

- 1. Is number odd?
- 2. Is number a power of 2?
- 3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Paste source code here, with a screenshot of a working application.

Source code:


```
import java.util.Scanner;
public class Main {
  public static void main(String[] args) {
    Scanner scanner = new Scanner(System.in);
    boolean exit = false;

    while (!exit) {
        System.out.println("\nMenu:");
        System.out.println("1. Is number odd?");
        System.out.println("2. Is number a power of 2?");
        System.out.println("3. Two's complement of number?");
        System.out.println("4. Exit");
```

```
System.out.print("Choose an option: ");
int choice = scanner.nextInt();
switch (choice) {
  case 1:
    System.out.print("Enter a number: ");
    int number1 = scanner.nextInt();
    if (isOdd(number1)) {
      System.out.println("The number " + number1 + " is odd.");
    } else {
      System.out.println("The number " + number1 + " is even.");
    }
    break;
  case 2:
    System.out.print("Enter a number: ");
    int number2 = scanner.nextInt();
    if (isPowerOfTwo(number2)) {
      System.out.println("The number " + number2 + " is a power of 2.");
    } else {
      System.out.println("The number " + number2 + " is not a power of 2.");
    }
    break;
  case 3:
    System.out.print("Enter a number: ");
    int number3 = scanner.nextInt();
    int complement = twosComplement(number3);
    System.out.println("The two's complement of " + number3 + " is " + complement + ".");
    break;
  case 4:
```

```
System.out.println("Exiting the program.");
         exit = true;
         break;
      default:
         System.out.println("Invalid choice. Please try again.");
    }
  }
  scanner.close();
}
// check if a number is odd
public static boolean isOdd(int number) {
  return (number & 1) != 0;
}
// check if a number is a power of 2
public static boolean isPowerOfTwo(int number) {
  return number > 0 && (number & (number - 1)) == 0;
}
// calculate the two's complement of a number
public static int twosComplement(int number) {
  return ~number + 1;
}
```

}

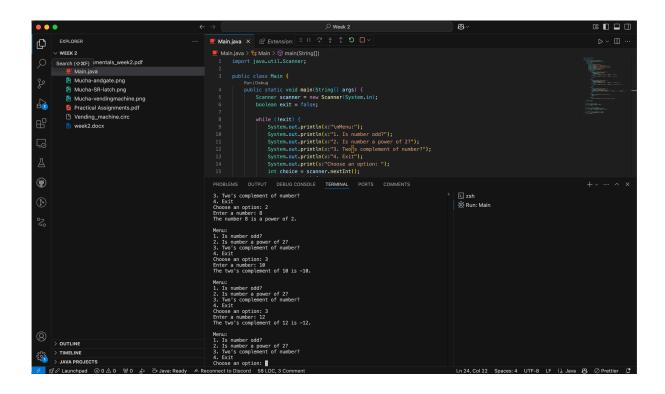

Ready? Then save this file and export it as a pdf file with the name: week2.pdf